

6.302 Feedback Systems

Recitation 11: Phase-locked Loops

Prof. Joel L. Dawson

Phase-locked loops are a foundational building block for analog circuit design, particularly for communications circuits. They provide a good example system for this class because they are an excellent exercise in physical modeling. In these systems, the key variable is the phase of a sinusoid. As a first step, then we must be precise about what we mean by the phase of a sinusoid. Consider:

$$v(t) = \cos [\phi(t)]$$

We define the frequency of a sinusoid as the instantaneous rate of change of its phase. That is:

$$\omega \equiv \frac{d\phi}{dt}$$

EXAMPLE: $v(t) = \cos (\omega_0 t + \phi_0)$

$$\text{PHASE} = \omega_0 t + \phi_0 = \phi(t)$$

$$\text{FREQUENCY} = \frac{d\phi(t)}{dt} = \omega_0$$

To be consistent, we write the phase in terms of the frequency:

$$\phi = \int_{-\infty}^t \omega(t) dt$$


So to understand phase-locked loops (PLLs) we must make the following conceptual jump...

6.302 Feedback Systems


Recitation 11: Phase-locked Loops

Prof. Joel L. Dawson


VOLTAGE PICTURE:

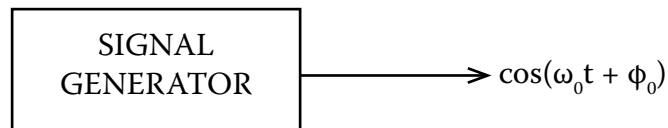

PLL PICTURE:

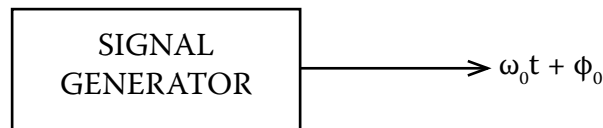

Now, the anatomy of a PLL:

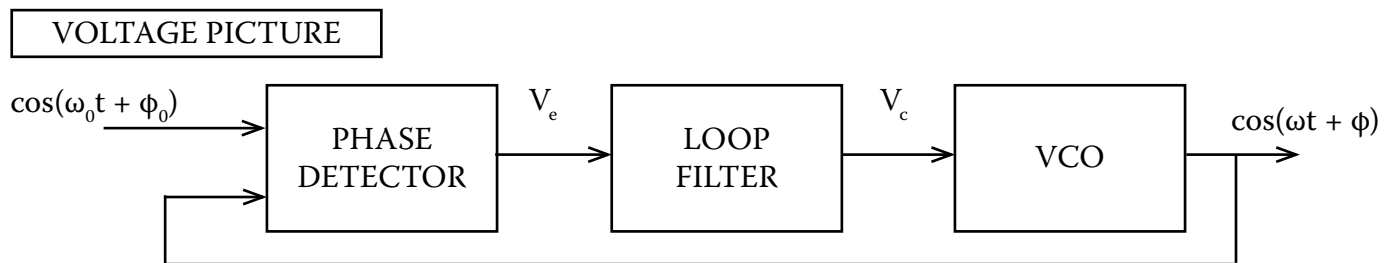

VCO = Voltage Controlled Oscillator

$$\omega = k_0 V_c$$


$$V_e = k_d (\phi_0 - \phi)$$

$$[k_d] = \text{V/RAD}$$

Notice, if V_e is constant, $\phi - \phi_0$ is constant $\Rightarrow \omega_0 = \omega$

A PLL locks the output of a VCO in frequency and phase to an incoming periodic signal.

PLL PICTURE

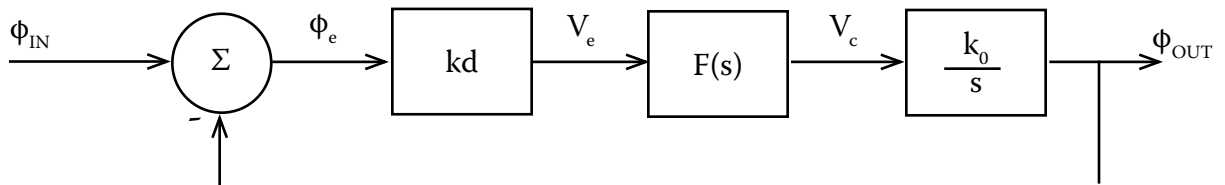

VCO is an integrator. Its output frequency is

$$\frac{d\phi_{\text{OUT}}}{dt} = k_0 V_c \Rightarrow \phi_{\text{OUT}} = \int_{-\infty}^t k_0 V_c dt$$


6.302 Feedback Systems

Recitation 11: Phase-locked Loops

Prof. Joel L. Dawson

Now, let's look at how we put together and use PLLs. To start, how does one build a phase detector?

1) ANALOG MULTIPLIER:

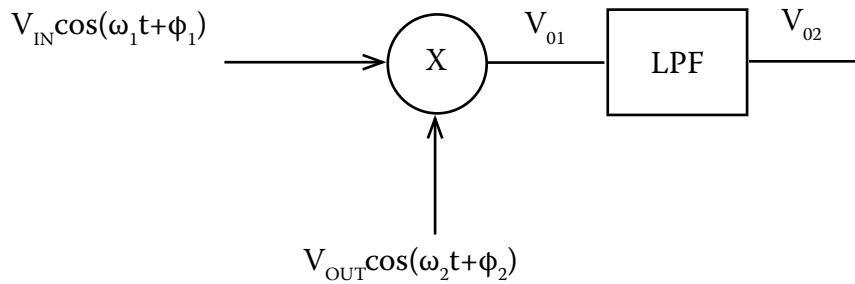

$$\begin{aligned}
 V_{01} &= V_{IN} V_{OUT} \cos(\omega_1 t + \phi_1) \cos(\omega_2 t + \phi_2) \\
 &= \frac{1}{2} V_{IN} V_{OUT} [\cos(\omega_1 t + \phi_1 + \omega_2 t + \phi_2) + \cos(\omega_1 t + \phi_1 - \omega_2 t - \phi_2)]
 \end{aligned}$$

IF $\omega_1 = \omega_2 = \omega$

$$\rightarrow V_{01} = \frac{1}{2} V_{IN} V_{OUT} [\cos(2\omega t + \phi_1 + \phi_2) + \cos(\phi_1 - \phi_2)]$$

After LPF, we lose high-frequency component:

$$V_{02} = \frac{1}{2} V_{IN} V_{OUT} [\cos(\phi_1 - \phi_2)]$$


So we get zero out of the phase detector when $\phi_1 - \phi_2 = \pm \pi/2$.

Linearizing about this condition, we would say:

$$\Delta V_{02} = \pm \underbrace{\frac{V_{IN} V_{OUT}}{2}}_{k_0} \Delta \phi$$

(Notice that the constant k_0 depends on the amplitude of the sinusoids.)

2) DIGITAL XOR GATE

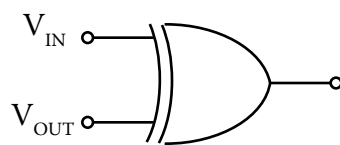


V_{IN}	V_{OUT}	V_{XOR}
0	0	0
0	1	1
1	0	1
1	1	0

6.302 Feedback Systems

Recitation 11: Phase-locked Loops

Prof. Joel L. Dawson

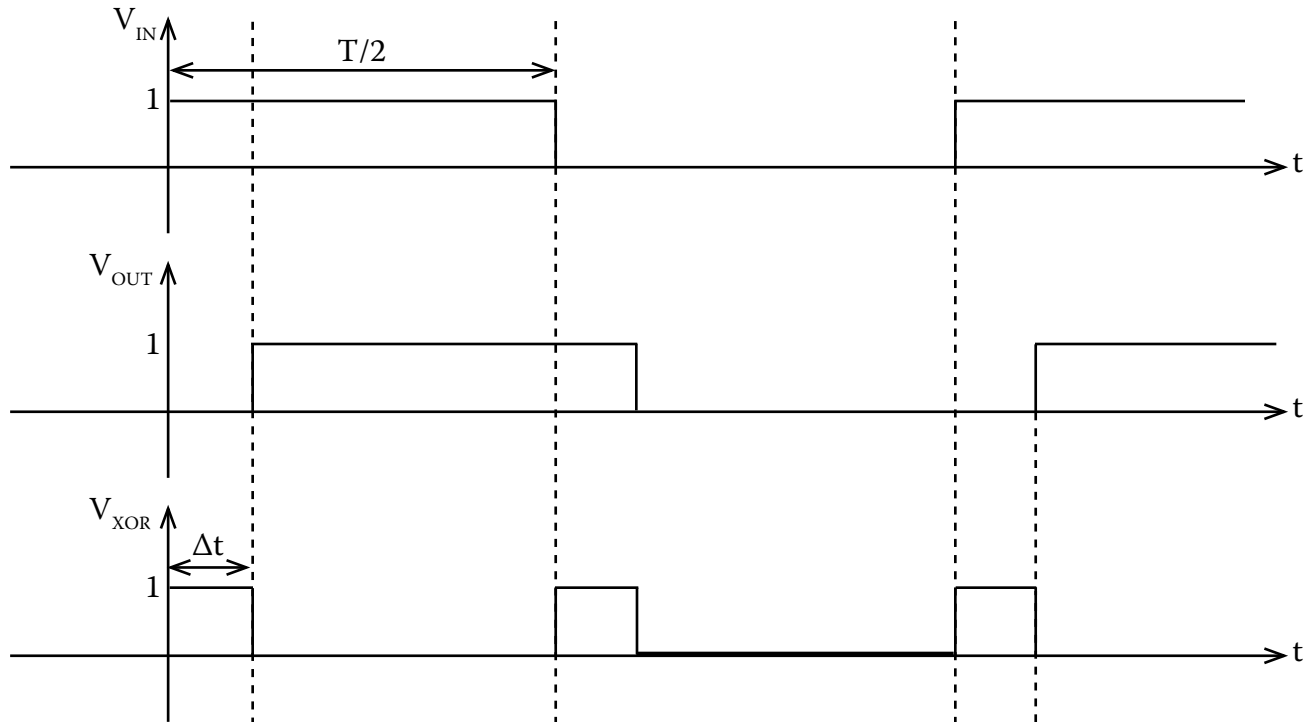Easiest to analyze in time domain. (Here, assume square wave inputs.)



For our phase detector output, we'll use the average (DC) value of V_{XOR} :

$$\overline{V}_{XOR} = \frac{1}{T/2} [1 \cdot \Delta t + 0 \cdot (T/2 - \Delta t)] = 2 \cdot \frac{\Delta t}{T}$$

Now, how do we relate this to phase? Recall that for a sinusoid:


$$\cos(\omega t - \phi) = \cos(2\pi f t - \phi)$$

$$= \cos\left(\frac{2\pi}{T} t - \phi\right)$$

$$= \cos\frac{2\pi}{T} \left(t - \frac{\phi}{2\pi} \cdot T\right)$$

$$= \cos\frac{2\pi}{T} (t - \Delta t) \Rightarrow \Delta t = \frac{\phi}{2\pi} \cdot T$$
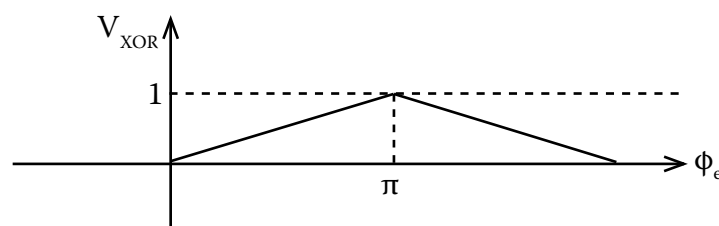
$$\text{THUS: } \overline{V}_{XOR} = \frac{2}{T} \left(\frac{\phi_e}{2\pi} \cdot T\right) = \frac{\phi_e}{2\pi}$$




6.302 Feedback Systems

Recitation 11: Phase-locked Loops

Prof. Joel L. Dawson

There are many other phase detectors, each with their own strengths and weaknesses. More on these later...

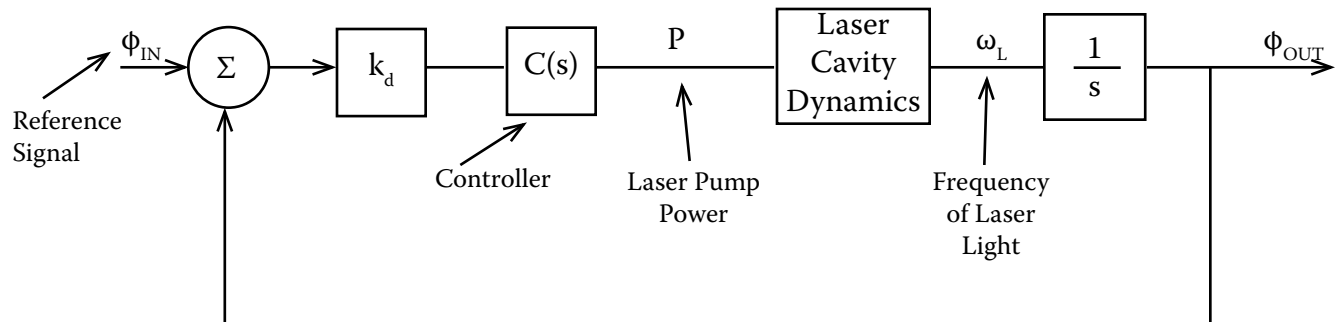Application to stabilization of the frequency of a laser



Locks frequency of laser light to a stable reference.

Typical laser cavity dynamics:

$$G(s) = \underbrace{e^{-sT}}_{\text{delay}} \underbrace{\frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}}_{\text{second order system}}$$

Typical choices for a controller:

$$C(s) = \frac{D_0 s}{D_0 s + P_0} \frac{I_0}{s}$$

Returning to a general case, we have $L(s) = \frac{k_0 k_d}{s} F(s)$, where as a designer you usually have some control over the form of $F(s)$. Suppose we choose $F(s) = 1$, so that $L(s)$ is just $\frac{k_0 k_d}{s}$. What is the steady-state error in response to a constant-frequency input?

$$\cos(\omega_0 t) \longrightarrow \text{ramp in phase} \longrightarrow \frac{\omega_0}{s^2}$$

6.302 Feedback Systems


Recitation 11: Phase-locked Loops

Prof. Joel L. Dawson

Steady-state error, then, is

$$\begin{aligned} \lim_{t \rightarrow \infty} \phi_e(t) &= \lim_{s \rightarrow 0} s \left[\frac{\omega_0}{s^2} \cdot \frac{1}{1+C(s)} \right] = \lim_{s \rightarrow 0} \frac{\omega_0}{s} \cdot \frac{1}{1 + \frac{k_0 k_d}{s}} \\ &= \frac{\omega_0}{k_0 k_d} \end{aligned}$$

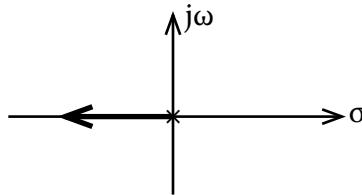=> Large $k_0 k_d$ for small phase error. But according to root locus,




Large $k_0 k_d$ also means large bandwidth. If we have a noisy reference, large bandwidth is not a good thing.

We can improve things by being more sophisticated in our choice of $F(s)$:

$$F(s) = \frac{1}{\tau s + 1} \quad \Rightarrow \quad L(s) = \frac{k}{s(\tau s + 1)}$$

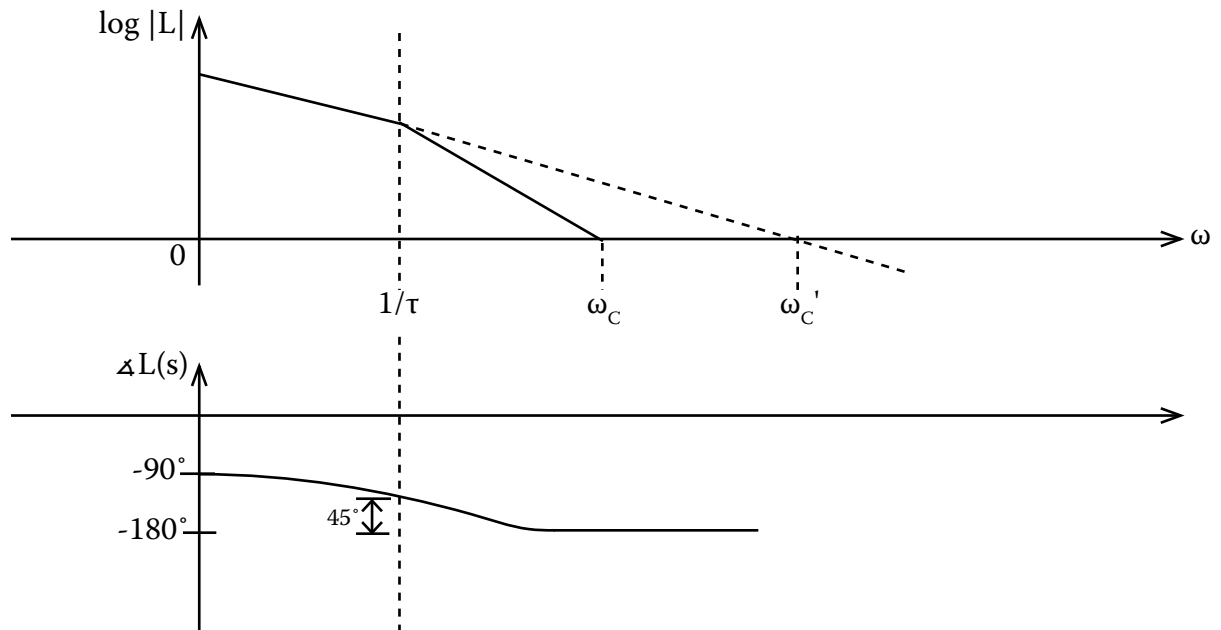Steady state error is still $\frac{\omega_0}{k}$, but bandwidth is reduced:




6.302 Feedback Systems

Recitation 11: Phase-locked Loops

Prof. Joel L. Dawson

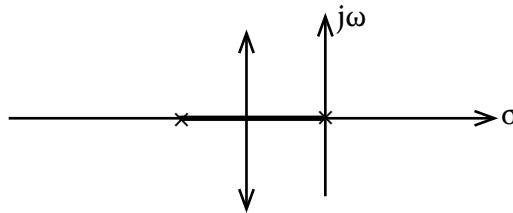Now we've got our improved noise performance, but increasing k will lower our damping ratio:



Put another way, increasing k will lower our phase margin.

=> we must decide what stability margins are acceptable in our application.

Suppose we decide that a 25% overshoot in the step response is acceptable. Using our chart of 2nd order parameters, we discover that this corresponds to $\zeta = 0.4$ and $M_p = 1.4$. This means we should design for a phase margin of

$$M_p \approx \frac{1}{\sin \phi_m}$$
$$\phi_m \approx \sin^{-1} \left(\frac{1}{M_p} \right) \approx 45^\circ$$

We arrange for this by ensuring that $|L| = 1$ at the frequency for which $\angle L(s) = -135^\circ$. Looking at our Bode Plot, we see that this frequency is just $\omega = 1/\tau$. On the asymptotic magnitude plot, $|L(s)|$ at this frequency is $\frac{k}{1/\tau} = k\tau$. The actual magnitude is $\frac{k\tau}{\sqrt{2}}$.

We therefore choose k using

$$\frac{k\tau}{\sqrt{2}} = 1 \Rightarrow k = \frac{\sqrt{2}}{\tau}$$