


# News

- Quiz #2: Monday, 3/14, 10AM
- Same procedure as for quiz 1
  - Review in class Fri, 3/11
  - **Evening review, Fri, 3/11**
  - 2 practice quizzes (+ practice problems)
  - Formula sheet
  - From Potential to Kirchoffs Rules, EF exp

Mar 9 2005

web.mit.edu/8.02x/www


# Demo

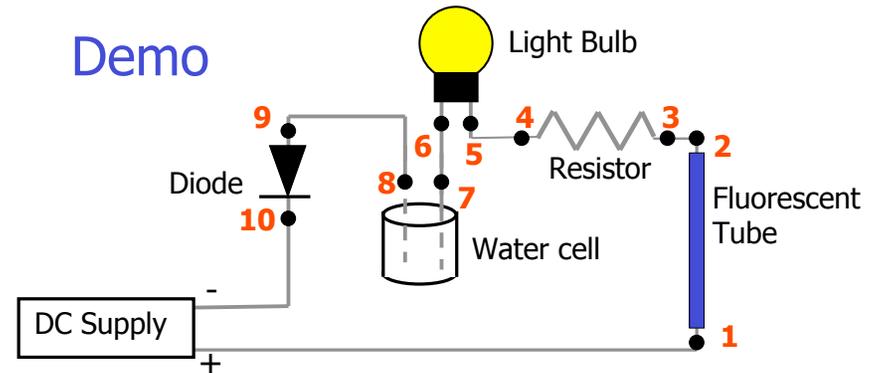

Mar 9 2005

web.mit.edu/8.02x/www

# Demo

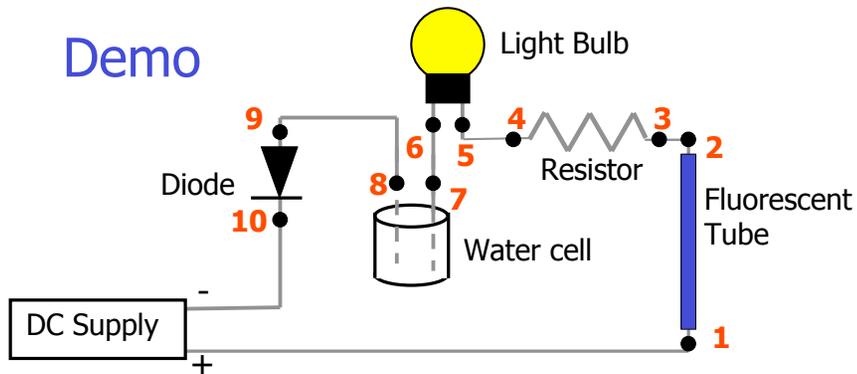


Output voltage  $V_{out} = V_{12} + V_{34} + V_{56} + V_{78} + V_{910}$

Mar 9 2005

web.mit.edu/8.02x/www

# Loop Rule

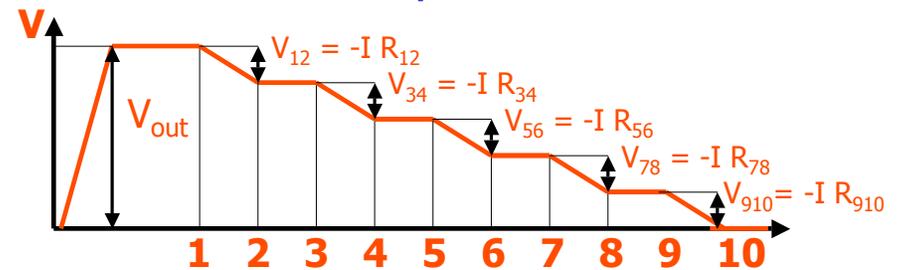

In general,  $\sum V_j = 0$  for any closed loop Loop Rule

Mar 9 2005

web.mit.edu/8.02x/www