

## **8.02x Electricity and Magnetism**

### **Problem Set 10**

**Issued:** Sun, April 17

**Due:** Fri, April 22, 4PM <- note Date & Time!

#### **Reading suggestions from Young & Freedman**

Mon, 4/18 Patriots day vacation

Wed, 4/20: AC Circuits, Inductors, RL Circuits 31.2, 30.2,30.4

Fri, 4/22: RLC circuits, Oscillations: 30.5, 30.6

#### **Problem 1 (6 points):**

Compare the oscillations of an LRC circuit to the vibration of a mass  $m$  on a spring. What do  $L$  and  $C$  correspond to in the mechanical system? What is the mechanical analog to  $R$ ?

#### **Problem 2(6 points)**

You have probably noticed that when a circuit carrying a large current is interrupted, a spark occurs between the poles of the switch (or the poles of a plug that is pulled).

- (a) Explain this phenomenon. Where does the energy for the spark come from?
- (b) Assume an inductor  $L=1\text{mH}$  and a resistor  $R=10\Omega$  are connected in series to a battery providing  $V=100\text{V}$ . How much energy is stored in the inductor a long time after the circuit is closed?.

**Problem 3 (6 points)** Young&Freedman, Problem 30.10

**Problem 4 (6 points)** Young&Freedman, Problem 30.14

**Problem 5 (6 points)** Young&Freedman, Problem 30.26